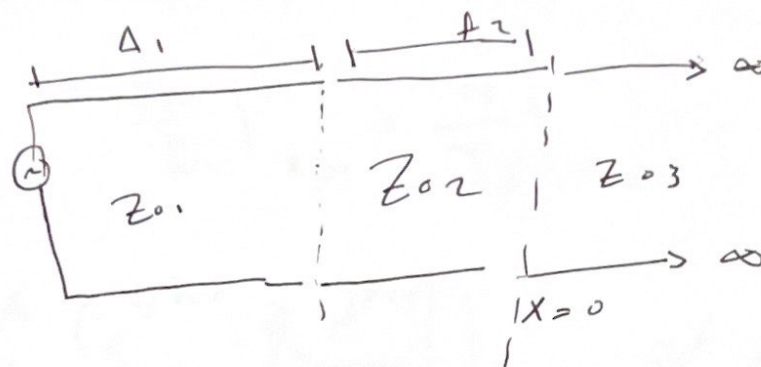


Homework 11
Nasser Alrasbi

11



$$Z_{02} = \frac{1}{2} Z_{01}$$

$$Z_{03} = \frac{1}{3} Z_{01}$$

$$\Delta = \Delta_1$$

$$\Delta_2 = \frac{3\lambda_c}{4}$$

$$\hat{V}_n(x) = \hat{V}_n^+ \left(e^{-j\beta_n x} + \tilde{\rho}_n e^{j\beta_n x} \right)$$

$$\hat{I}_n(x) = \frac{\hat{V}_n^+}{Z_{0n}} \left(e^{-j\beta_n x} - \tilde{\rho}_n e^{j\beta_n x} \right)$$

- Since region 3 goes to ∞ , we assume that there is no wave traveling in the $-x$ direction

Region 3

$$\tilde{V}_3 = \tilde{V}_3^+ (e^{-j\beta_3 x}) \quad \tilde{I}_3 = \frac{\tilde{V}_3^+}{Z_{03}} (e^{-j\beta_3 x})$$

Region 2

$$\tilde{V}_2 = \tilde{V}_2^+ \left(e^{-j\beta_2 x} + \tilde{\rho}_2 e^{j\beta_2 x} \right)$$

$$\tilde{I}_2 = \frac{\tilde{V}_2^+}{Z_{02}} \left(e^{-j\beta_2 x} - \tilde{\rho}_2 e^{j\beta_2 x} \right)$$

Region 1

$$\tilde{V}_1(x) = \tilde{V}_1^+ \left(e^{-j\beta_1 x} + \tilde{\rho}_1 e^{j\beta_1 x} \right)$$

$$\tilde{I}_1(x) = \frac{\tilde{V}_1^+}{Z_{01}} \left(e^{-j\beta_1 x} - \tilde{\rho}_1 e^{j\beta_1 x} \right)$$

- Apply boundary conditions at the 2 and 3 interface

$$V_2(x=0) = V_3(x=0)$$

$$I_2(x=0) = I_3(x=0)$$

$$\frac{V_2}{I_2} \Big|_{x=0} = \frac{V_3}{I_3} \Big|_{x=0}$$

$$\frac{\cancel{\tilde{V}_2} (e^{-j\beta_2 x} + \hat{P}_2 e^{j\beta_2 x})}{\cancel{\tilde{I}_2} (e^{-j\beta_2 x} - \hat{P}_2 e^{j\beta_2 x})} \Big|_{x=0} = \frac{\cancel{\tilde{V}_3} e^{-j\beta_3 x}}{\cancel{\tilde{I}_3} e^{-j\beta_3 x}} \Big|_{x=0}$$

$$\frac{Z_{02} (1 + \hat{P}_2)}{1 - \hat{P}_2} = Z_{03}$$

$$Z_{02} (1 + \hat{P}_2) = Z_{03} (1 - \hat{P}_2)$$

$$Z_{02} + Z_{02} \hat{P}_2 = Z_{03} - Z_{03} \hat{P}_2$$

$$\hat{P}_2 + Z_{03} \hat{P}_2 = Z_{03} - Z_{02}$$

$$\boxed{\hat{P}_2 = \frac{Z_{03} - Z_{02}}{Z_{02} + Z_{03}}}$$

$$\hat{P}_2 = \frac{\frac{1}{3} Z_{01} - \frac{1}{2} Z_{01}}{\frac{1}{2} Z_{01} + \frac{1}{3} Z_{01}} = \frac{\frac{1}{3} - \frac{1}{2}}{\frac{1}{2} + \frac{1}{3}} = \frac{2-3}{3+2} = -\frac{1}{5}$$

$$\boxed{\hat{P}_2 = -\frac{1}{5}}$$

- Boundary conditions at the interface of region 1 and 2
 $x = -\Delta_2 = -\frac{3}{4}\lambda$

$$\left. \frac{\tilde{V}_1^+ (e^{-jB_1 x} + \tilde{\rho}_1 e^{jB_1 x})}{\frac{1}{Z_{01}} (e^{-jB_1 x} - \tilde{\rho}_1 e^{jB_1 x})} \right|_{x=\Delta_2} = \left. \frac{\tilde{V}_2^+ (e^{-jB_2 x} + \tilde{\rho}_2 e^{jB_2 x})}{\frac{1}{Z_{02}} (e^{-jB_2 x} - \tilde{\rho}_2 e^{jB_2 x})} \right|_{x=-\Delta_2}$$

$$\frac{Z_{01} (e^{+jB_1 \Delta_2} + \tilde{\rho}_1 e^{-jB_1 \Delta_2})}{e^{+jB_1 \Delta_2} - \tilde{\rho}_1 e^{-jB_1 \Delta_2}} = \frac{Z_{02} (e^{+jB_2 \Delta_2} + \tilde{\rho}_2 e^{-jB_2 \Delta_2})}{e^{+jB_2 \Delta_2} - \tilde{\rho}_2 e^{-jB_2 \Delta_2}}$$

$$\left[Z_{02} = \frac{1}{2} Z_{01} \quad \tilde{\rho}_2 = -\frac{1}{5} \quad B_2 \Delta_2 = \frac{2\pi}{\lambda_2} \frac{3\lambda_2}{4} = \frac{3\pi}{4} \right]$$

$$\frac{Z_{01} e^{+jB_1 \Delta_2} (1 + \tilde{\rho}_1 e^{-2jB_1 \Delta_2})}{e^{+jB_1 \Delta_2} (1 - \tilde{\rho}_1 e^{-2jB_1 \Delta_2})} = \frac{\frac{1}{2} Z_{01} (-i + (-\frac{1}{5})i)}{-i - (-\frac{1}{5})i}$$

$$\frac{(1 + \tilde{\rho}_1 e^{-2jB_1 \Delta_2})}{(1 - \tilde{\rho}_1 e^{-2jB_1 \Delta_2})} = \frac{\frac{1}{2} i \left(\frac{-1 - \frac{1}{5}}{-1 + \frac{1}{5}} \right)}{\frac{1}{2} \frac{(-5-1)}{(-5+1)}} = \frac{1}{2} \frac{(-6)}{(-4)} = \frac{3}{4}$$

$$1 + \tilde{\rho}_1 e^{-2jB_1 \Delta_2} = \frac{3}{4} + \frac{3}{4} \tilde{\rho}_1 e^{-2jB_1 \Delta_2}$$

$$\tilde{\rho}_1 (e^{-2jB_1 \Delta_2} + \frac{3}{4} e^{-2jB_1 \Delta_2}) = \frac{3}{4} - 1 = -\frac{1}{4}$$

$$\tilde{\rho}_1 = \frac{-1}{4 e^{-2jB_1 \Delta_2} (1 + \frac{3}{4})} = -\frac{1}{7} e^{2jB_1 \Delta_2}$$

$$\hat{p}_1 = -\frac{1}{7} e^{2j B \cdot \Delta z}$$

$$\lambda_1 = 10 \text{ cm}, \lambda_2 = 5 \text{ cm}, \frac{\lambda_1}{\lambda_2} = 2$$

$$B \cdot \Delta z = \frac{2\pi}{\lambda_1} \frac{3\lambda_2}{4} = \frac{3\pi}{2} \frac{\lambda_2}{\lambda_1} = \frac{3\pi}{4}$$

$$\hat{p}_1 = -\frac{1}{7} e^{2j \frac{3\pi}{4}} = -\frac{1}{7} e^{j \frac{3\pi}{2}} = -\frac{1}{7} (-j) = \boxed{\frac{1}{7} j = \hat{p}_1}$$

- Solve for amplitudes \hat{V}_1^+ , \hat{V}_2^+ , \hat{V}_3^+

$$\boxed{\hat{V}_1^+ = \hat{V}_s}$$

The right region (1) has the amplitude of the source \hat{V}_s

- at $x = -A_2$ boundary

$$\hat{V}_1(x = -A_2) = \hat{V}_2(x = -A_2)$$

$$\hat{V}_1^+ (e^{-jB_1 x} + \hat{P}_1 e^{jB_1 x}) \Big|_{x=-A_2} = \hat{V}_2^+ (e^{-jB_2 x} + \hat{P}_2 e^{jB_2 x}) \Big|_{x=-A_2}$$

$$\left[\begin{array}{l} \hat{V}_1^+ = \hat{V}_s \\ \hat{P}_1 = \frac{j}{7} \end{array} \right] \quad \hat{P}_2 = -\frac{1}{5}$$

$$\hat{V}_s (e^{jB_1 A_2} + \frac{j}{7} e^{-jB_1 A_2}) = \hat{V}_2^+ (e^{jB_2 A_2} - \frac{1}{5} e^{-jB_2 A_2})$$

$$\left[\begin{array}{l} B_1 A_2 = \frac{2\pi}{\lambda_1} \frac{3\lambda_2}{4} = \frac{3\pi}{2} \frac{5}{10} = \frac{3\pi}{4} \quad B_2 A_2 = \frac{2\pi}{\lambda_2} \frac{3\lambda_2}{4} = \frac{3\pi}{2} \end{array} \right]$$

$$\hat{V}_s (e^{j\frac{3\pi}{4}} + \frac{j}{7} e^{-j\frac{3\pi}{4}}) = \hat{V}_2^+ (e^{j\frac{3\pi}{2}} - \frac{1}{5} e^{-j\frac{3\pi}{2}})$$

$$\hat{V}_s \left[\left(\frac{1}{\sqrt{2}} + \frac{j}{7} \right) + \frac{j}{7} \left(\frac{1}{\sqrt{2}} - \frac{j}{\sqrt{2}} \right) \right] = \hat{V}_2^+ (-j - \frac{1}{5} j)$$

$$\frac{\hat{V}_s}{\sqrt{2}} \left[-1 + j - \frac{j}{7} + \frac{1}{7} \right] = -\frac{6j}{5} \hat{V}_2^+$$

$$\tilde{V}_2^+ = \left(\frac{-S}{6j} \right) \frac{\hat{V}_S}{\sqrt{2}} \left(\frac{6j}{1} - \frac{6}{1} \right) = \frac{-S}{7\sqrt{2}} \hat{V}_S (j-1) \left(\frac{j}{j} \right)$$

$$\tilde{V}_2^+ = \frac{S}{7\sqrt{2}} \hat{V}_S (-1-j)$$

$$\boxed{\hat{V}_2^+ = \frac{-S}{7\sqrt{2}} \hat{V}_S (1+j)}$$

$\Rightarrow x=0$ Boundary

$$\hat{V}_2(x=0) = \hat{V}_3(x=0)$$

$$\tilde{V}_2^+ \left(e^{-j\beta_2 x} - \frac{1}{S} e^{j\beta_2 x} \right) = \tilde{V}_3^+ e^{-j\beta_3 x} \Big|_{x=0}$$

$$\hat{V}_2^+ \left(1 - \frac{1}{S} \right) = \tilde{V}_3^+$$

$$\tilde{V}_3^+ = \left(\frac{4}{8} \right) \left(\frac{-S}{7\sqrt{2}} \hat{V}_S (1+j) \right)$$

$$\boxed{\tilde{V}_3^+ = \frac{-4}{7\sqrt{2}} \hat{V}_S (1+j)}$$

2

$$\tilde{p}_2 = \frac{\frac{Z_{o3}}{Z_{o2}} - 1}{\frac{Z_{o3}}{Z_{o2}} + 1} \Rightarrow \frac{Z_{o3}}{Z_{o2}} = \frac{1/3}{1/2} = \frac{2}{3} + 0j$$

from smith chart

$$\boxed{\tilde{p}_2 = -\frac{1}{5}}$$

$$\tilde{p}_1 = \frac{\frac{Z_{o2}}{Z_{o1}} - 1}{\frac{Z_{o2}}{Z_{o1}} + 1} \Rightarrow \frac{Z_{o2}}{Z_{o1}} = \frac{1/2}{1} = \frac{1}{2} + 0j$$

from smith chart

$$\boxed{\tilde{p}_1 = \frac{1}{3}}$$

7